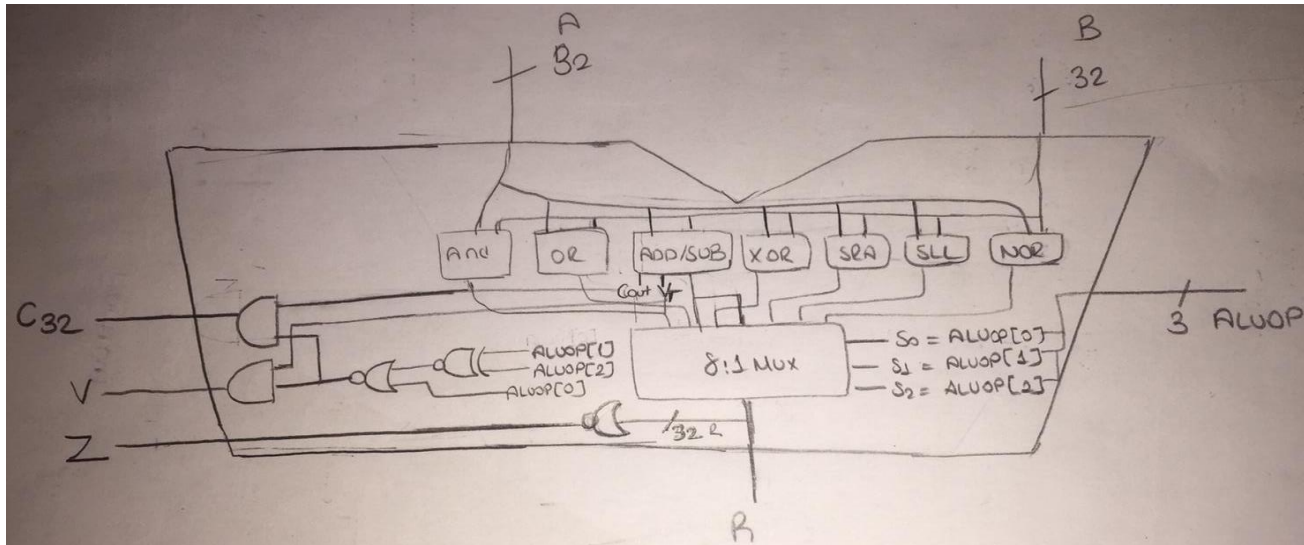


# CSE 331 Computer Organization

## Project 2 – ALU with Structural Verilog

SEVGİ BAYANSALDUZ – 151044076

The first thing I did was to design the module alu32. Schematic design for the module **alu32**:



The module **alu32** and its description:

```
module alu32(R,C32,V,Z,A,B,ALUOP);
    output [31:0]R;
    output V,C32,Z;
    input [31:0] A,B;
    input [2:0] ALUOP;

    wire [31:0] andd,orr,add_sub,xorr,sll,sra,norr;
    wire C,overflow,steat,nott,temp;

    and_32bit aluand(andd,A,B);
    or_32bit aluor(orr,A,B);
    adder_subtractor_32_bit op3_5(add_sub,C,overflow,A,B,ALUOP);
    xor_32bit aluxor(xorr,A,B);
    shift_right_arithmetic alusra(sra,A,B[4:0],ALUOP[0]);
    shift_left_logical alusll(sll,A,B[4:0],ALUOP[0]);
    nor_32bit alunor(norr,A,B);

    //Result is seted
    mux_8_1 alumux(R,andd,orr,add_sub,xorr,add_sub,sra,sll,norr,ALUOP);
    //Z is seted
    nor(Z,R[0],R[1],R[2],R[3],R[4],R[5],R[6],R[7],R[8],R[9],R[10],R[11],R[12],
    R[13],R[14],R[15],R[16],R[17],R[17],R[17],R[17],R[18],R[19],R[20],R[21],R[22],R[23],R[24],
    R[25],R[26],R[27],R[28],R[29],R[30],R[31]);

    //Setting of V
    xnor(temp,ALUOP[2],ALUOP[1]);
    nor(steat,temp,ALUOP[0]);

    and(V,steat,overflow); // v is setted in this step
    //Setting of C32
    and(C32,steat,C); //C32 is setted in this step

endmodule // end of module
```

The module requests three inputs: two 32 bits number, and a 3bits alu operation's code. And returns a 32bits number, a zero bit, a overflow bit and a carry out bit.

This module calls the modules shown in the above picture one by one. And then saves their results in the wires.


Then sends these wires to the 8:1 multiplexer to get the R(Result) according to the alu operation's code.

After R is set, this module calculates Zero bit .If one or more bits in the Result number is equal to 1,This bit will be 0, otherwise will be 1.


If alu operation's code is 100 or 010(sub or add),steat will be 1,otherwise will be 0.

After state is set, C32 and V will be set; if state is 1 and the wire C/overflow is 1,C/overflow will be 1,otherwise will be 0.

 The schematic design of the steat is in the side picture.



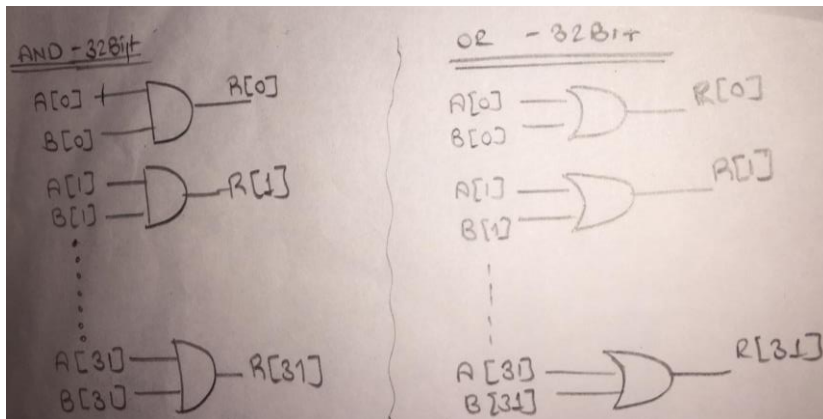After the design of the module alu32, I designed the modules 32 bit and/or/xor/nor. Schematic design for some modules.





```
module or_32bit(orr,A,B);
output [31:0] orr;
input [31:0] A,B;

or(orr[0],A[0],B[0]), (orr[1],A[1],B[1]), (orr[2],A[2],B[2]), (orr[3],A[3],B[3]), (orr[4],A[4],B[4]), (orr[5],A[5],B[5]),
(orr[6],A[6],B[6]), (orr[7],A[7],B[7]), (orr[8],A[8],B[8]), (orr[9],A[9],B[9]), (orr[10],A[10],B[10]), (orr[11],A[11],B[11]),
(orr[12],A[12],B[12]), (orr[13],A[13],B[13]), (orr[14],A[14],B[14]), (orr[15],A[15],B[15]), (orr[16],A[16],B[16]), (orr[17],A[17],B[17]),
(orr[18],A[18],B[18]), (orr[19],A[19],B[19]), (orr[20],A[20],B[20]), (orr[21],A[21],B[21]), (orr[22],A[22],B[22]), (orr[23],A[23],B[23]),
(orr[24],A[24],B[24]), (orr[25],A[25],B[25]), (orr[26],A[26],B[26]), (orr[27],A[27],B[27]), (orr[28],A[28],B[28]), (orr[29],A[29],B[29]),
(orr[30],A[30],B[30]), (orr[31],A[31],B[31]);

endmodule//end of module
```

The modules 32 bit and,or,xor are same like the module 32 bit or.

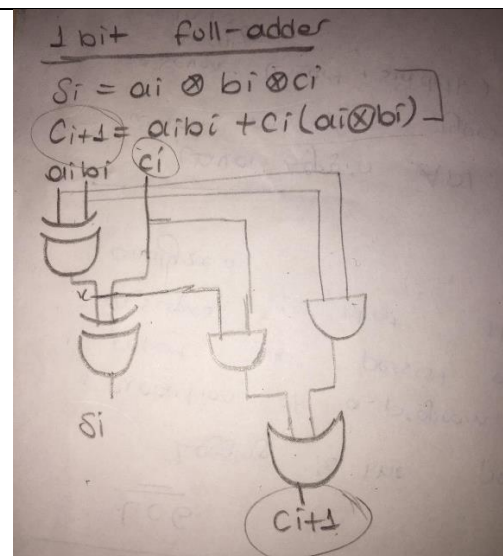 Then I designed the module adder\_subtractor\_32\_bit. Schematic design of this module is the below:



```
module full_adder_1_bit(Res,Cout,A,B,Cin);
output Res,Cout;
input A,B,Cin;
wire abxor,abc,ab;

xor (abxor,A,B);
xor (Res,abxor,Cin); //Res is seted

and(abc,abxor,Cin);
and(ab,A,B);
or(Cout,abc,ab); //Cout is seted

endmodule// end of module
```

The mdule full adder, I wirted according to above picture.

```

module adder_subtractor_32_bit(Res,C32,V,A,B,ALUOP);

output [31:0] Res;
output C32,V;
input [31:0] A,B;
input [2:0] ALUOP;
wire[31:0] b,C;

xor(b[0],B[0],ALUOP[2]),(b[1],B[1],ALUOP[2]),(b[2],B[2],ALUOP[2]),(b[3],B[3],ALUOP[2]),(b[4],B[4],ALUOP[2]),(b[5],B[5],ALUOP[2]),(b[6],B[6],ALUOP[2]),(b[7],B[7],ALUOP[2]),(b[8],B[8],ALUOP[2]),(b[9],B[9],ALUOP[2]),(b[10],B[10],ALUOP[2]),(b[11],B[11],ALUOP[2]),(b[12],B[12],ALUOP[2]),(b[13],B[13],ALUOP[2]),(b[14],B[14],ALUOP[2]),(b[15],B[15],ALUOP[2]),(b[16],B[16],ALUOP[2]),(b[17],B[17],ALUOP[2]),(b[18],B[18],ALUOP[2]),(b[19],B[19],ALUOP[2]),(b[20],B[20],ALUOP[2]),(b[21],B[21],ALUOP[2]),(b[22],B[22],ALUOP[2]),(b[23],B[23],ALUOP[2]),(b[24],B[24],ALUOP[2]),(b[25],B[25],ALUOP[2]),(b[26],B[26],ALUOP[2]),(b[27],B[27],ALUOP[2]),(b[28],B[28],ALUOP[2]),(b[29],B[29],ALUOP[2]),(b[30],B[30],ALUOP[2]),(b[31],B[31],ALUOP[2]);

full_adder_1_bit f1(Res[0],C[1],A[0],b[0],ALUOP[2]);
full_adder_1_bit f2(Res[1],C[2],A[1],b[1],C[1]);
full_adder_1_bit f3(Res[2],C[3],A[2],b[2],C[2]);
full_adder_1_bit f4(Res[3],C[4],A[3],b[3],C[3]);
full_adder_1_bit f5(Res[4],C[5],A[4],b[4],C[4]);
full_adder_1_bit f6(Res[5],C[6],A[5],b[5],C[5]);
full_adder_1_bit f7(Res[6],C[7],A[6],b[6],C[6]);
full_adder_1_bit f8(Res[7],C[8],A[7],b[7],C[7]);
full_adder_1_bit f9(Res[8],C[9],A[8],b[8],C[8]);
full_adder_1_bit f10(Res[9],C[10],A[9],b[9],C[9]);
full_adder_1_bit f11(Res[10],C[11],A[10],b[10],C[10]);
full_adder_1_bit f12(Res[11],C[12],A[11],b[11],C[11]);
full_adder_1_bit f13(Res[12],C[13],A[12],b[12],C[12]);
full_adder_1_bit f14(Res[13],C[14],A[13],b[13],C[13]);
full_adder_1_bit f15(Res[14],C[15],A[14],b[14],C[14]);
full_adder_1_bit f16(Res[15],C[16],A[15],b[15],C[15]);
full_adder_1_bit f17(Res[16],C[17],A[16],b[16],C[16]);
full_adder_1_bit f18(Res[17],C[18],A[17],b[17],C[17]);
full_adder_1_bit f19(Res[18],C[19],A[18],b[18],C[18]);
full_adder_1_bit f20(Res[19],C[20],A[19],b[19],C[19]);
full_adder_1_bit f21(Res[20],C[21],A[20],b[20],C[20]);
full_adder_1_bit f22(Res[21],C[22],A[21],b[21],C[21]);
full_adder_1_bit f23(Res[22],C[23],A[22],b[22],C[22]);
full_adder_1_bit f24(Res[23],C[24],A[23],b[23],C[23]);
full_adder_1_bit f25(Res[24],C[25],A[24],b[24],C[24]);
full_adder_1_bit f26(Res[25],C[26],A[25],b[25],C[25]);
full_adder_1_bit f27(Res[26],C[27],A[26],b[26],C[26]);
full_adder_1_bit f28(Res[27],C[28],A[27],b[27],C[27]);
full_adder_1_bit f29(Res[28],C[29],A[28],b[28],C[28]);
full_adder_1_bit f30(Res[29],C[30],A[29],b[29],C[29]);
full_adder_1_bit f31(Res[30],C[31],A[30],b[30],C[30]);
full_adder_1_bit f32(Res[31],C32,A[31],b[31],C[31]);

xor(V,C32,C[31]); //overflow detector
endmodule //end of module

```

This module requests three inputs: two 32 bits number, and a 3bits alu operation's code. And returns a 32bits number, a overflow bit and a carry out bit.


First thing, number B and aluOp[2] (if this bit is 1,this module will make subtraction ,otherwise will make addition) is sent to the xor, and the return value is set to array b.

Then the bits of these two number will be sent to the module full\_adder\_1\_bit, according to the above schematic design.

V will set according to the schematic design.

The schematic design of the module shift\_left\_logical (sll)and shift\_right\_arithmetic(sra):

 The purple writings represent sll and the pink writings represent sra.





```

module shift_left_logical(Res,A,Select,op):
output [31:0]Res;
input [31:0] A;
input [4:0] Select;
input op;

wire [31:0] Temp1,Temp2,Temp3,Temp4;
//2^0 için kaydırma ->0
mux_2_1_lbit m1(Temp1[0],A[0],op,Select[0]);
mux_2_1_lbit m2(Temp1[1],A[1],A[0],Select[0]);
mux_2_1_lbit m3(Temp1[2],A[2],A[1],Select[0]);
mux_2_1_lbit m4(Temp1[3],A[3],A[2],Select[0]);
mux_2_1_lbit m5(Temp1[4],A[4],A[3],Select[0]);
mux_2_1_lbit m6(Temp1[5],A[5],A[4],Select[0]);
mux_2_1_lbit m7(Temp1[6],A[6],A[5],Select[0]);
mux_2_1_lbit m8(Temp1[7],A[7],A[6],Select[0]);
mux_2_1_lbit m9(Temp1[8],A[8],A[7],Select[0]);
mux_2_1_lbit m10(Temp1[9],A[9],A[8],Select[0]);
mux_2_1_lbit m11(Temp1[10],A[10],A[9],Select[0]);
mux_2_1_lbit m12(Temp1[11],A[11],A[10],Select[0]);
mux_2_1_lbit m13(Temp1[12],A[12],A[11],Select[0]);
mux_2_1_lbit m14(Temp1[13],A[13],A[12],Select[0]);
mux_2_1_lbit m15(Temp1[14],A[14],A[13],Select[0]);
mux_2_1_lbit m16(Temp1[15],A[15],A[14],Select[0]);
mux_2_1_lbit m17(Temp1[16],A[16],A[15],Select[0]);
mux_2_1_lbit m18(Temp1[17],A[17],A[16],Select[0]);
mux_2_1_lbit m19(Temp1[18],A[18],A[17],Select[0]);
mux_2_1_lbit m20(Temp1[19],A[19],A[18],Select[0]);
mux_2_1_lbit m21(Temp1[20],A[20],A[19],Select[0]);
mux_2_1_lbit m22(Temp1[21],A[21],A[20],Select[0]);
mux_2_1_lbit m23(Temp1[22],A[22],A[21],Select[0]);
mux_2_1_lbit m24(Temp1[23],A[23],A[22],Select[0]);
mux_2_1_lbit m25(Temp1[24],A[24],A[23],Select[0]);
mux_2_1_lbit m26(Temp1[25],A[25],A[24],Select[0]);
mux_2_1_lbit m27(Temp1[26],A[26],A[25],Select[0]);
mux_2_1_lbit m28(Temp1[27],A[27],A[26],Select[0]);
mux_2_1_lbit m29(Temp1[28],A[28],A[27],Select[0]);
mux_2_1_lbit m30(Temp1[29],A[29],A[28],Select[0]);
mux_2_1_lbit m31(Temp1[30],A[30],A[29],Select[0]);
mux_2_1_lbit m32(Temp1[31],A[31],A[30],Select[0]);
////////////////////////////////////





//2^1 için kaydırma
mux_2_1_lbit u1(Temp2[0],Temp1[0],op,Select[1]);
mux_2_1_lbit u2(Temp2[1],Temp1[1],op,Select[1]);
mux_2_1_lbit u3(Temp2[2],Temp1[2],Temp1[0],Select[1]);

```

I wrote the the sra and sll modules according to their schematic design. This module sends the bit  $A[i]$  to mux with select bit and  $op/A[i-1]$  (according to the schematic design. )

There is 5 select bit because this module takes a 32bits number.

  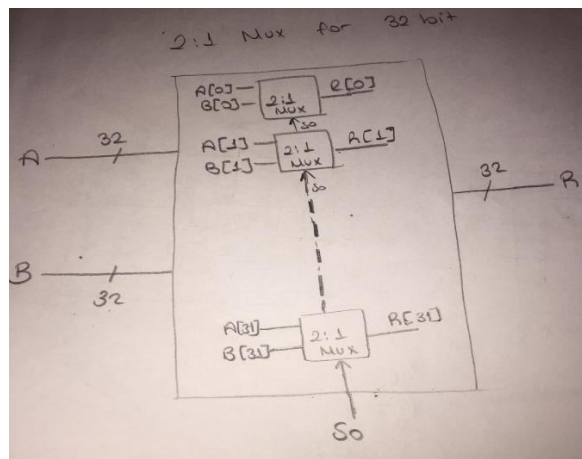 After designing of the operation modules, I designed and wrote modules for the multiplexer.Schematic designs:



```

module mux_2_1_1bit(Z,A,B,S0):
    output Z;
    input A,B,S0;

    wire aSnot,bs,notS0;

    and(bs,B,S0);

    not(notS0,S0);
    and(aSnot,notS0,A);

    or(Z,aSnot,bs);
endmodule// end of module

```

First I created 2:1 mux for one bit according to the schematic design.

```

module mux_2_1_32bit(Z,A,B,S0):
    output [31:0] Z;
    input [31:0] A,B;
    input S0;

    mux_2_1_1bit mux2_1(Z[0],A[0],B[0],S0);
    mux_2_1_1bit mux2_2(Z[1],A[1],B[1],S0);
    mux_2_1_1bit mux2_3(Z[2],A[2],B[2],S0);
    mux_2_1_1bit mux2_4(Z[3],A[3],B[3],S0);
    mux_2_1_1bit mux2_5(Z[4],A[4],B[4],S0);
    mux_2_1_1bit mux2_6(Z[5],A[5],B[5],S0);
    mux_2_1_1bit mux2_7(Z[6],A[6],B[6],S0);
    mux_2_1_1bit mux2_8(Z[7],A[7],B[7],S0);
    mux_2_1_1bit mux2_9(Z[8],A[8],B[8],S0);
    mux_2_1_1bit mux2_10(Z[9],A[9],B[9],S0);
    mux_2_1_1bit mux2_11(Z[10],A[10],B[10],S0);
    mux_2_1_1bit mux2_12(Z[11],A[11],B[11],S0);
    mux_2_1_1bit mux2_13(Z[12],A[12],B[12],S0);
    mux_2_1_1bit mux2_14(Z[13],A[13],B[13],S0);
    mux_2_1_1bit mux2_15(Z[14],A[14],B[14],S0);
    mux_2_1_1bit mux2_16(Z[15],A[15],B[15],S0);
    mux_2_1_1bit mux2_17(Z[16],A[16],B[16],S0);
    mux_2_1_1bit mux2_18(Z[17],A[17],B[17],S0);
    mux_2_1_1bit mux2_19(Z[18],A[18],B[18],S0);
    mux_2_1_1bit mux2_20(Z[19],A[19],B[19],S0);
    mux_2_1_1bit mux2_21(Z[20],A[20],B[20],S0);

```

Then I created 2:1 mux for 32 bits number. This module calls the module 2:1 mux for one bit 32 times.

```

module mux_4_1(Z,A,B,C,D,S0,S1):
    output [31:0] Z;
    input [31:0] A,B,C,D;
    input S0,S1;
    wire [31:0] wire1,wire2;

    mux_2_1_32bit m1(wire1,A,B,S0);
    mux_2_1_32bit m2(wire2,C,D,S0);
    mux_2_1_32bit m3(Z,wire1,wire2,S1); //output Z

endmodule//end of module

```

This module uses three 2:1 multiplexers.

```

module mux_8_1(Z,A,B,C,D,E,F,G,H,S):
    output [31:0] Z;
    input [31:0] A,B,C,D,E,F,G,H;
    input [2:0] S;

    wire [31:0] w1,w2;

    mux_4_1 m4_1(w1,A,B,C,D,S[0],S[1]);
    mux_4_1 m4_2(w2,E,F,G,H,S[0],S[1]);

    mux_2_1_32bit mresult(Z,w1,w2,S[2]); //output Z
endmodule// end of module

```

This module uses two 4:1 multiplexers and 1 2:1 multiplexer.

**1.**

**2.**

### 3.

```

# time = 0, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=000, Result=0000000000000000011100000000000, C32=0, V=0, Z=0
# time = 30, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=001, Result=11111111111111000111111111111111, C32=0, V=0, Z=0
# time = 60, A = 00000000000000000000001111111111110, B=1111111111111100011100000000001, ALUOP=010, Result=111111111111110011011111111111, C32=0, V=0, Z=0
# time = 90, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=011, Result=111111111111110000011111111111, C32=0, V=0, Z=0
# time = 120, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=100, Result=00000000000000100000011111111101, C32=0, V=0, Z=0
# time = 150, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=101, Result=10000000000000000001111111111111, C32=0, V=0, Z=0
# time = 180, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=110, Result=000000000000000111111111111100, C32=0, V=0, Z=0
# time = 210, A = 00000000000000000000111111111111110, B=1111111111111100011100000000001, ALUOP=111, Result=0000000000000001110000000000000, C32=0, V=0, Z=0

```